

MAKE A COPY OF THIS SHEET	Instruction Metadata				ROM Input [1]		Control Signals											ROM Output [2]
Instruction	Type	Opcode	Funct3	Funct7	Binary	Decimal	addi is provided as an example											Hex
							RegWEn	ImmSel	BrUn	ASel	BSel	ALUSel	MemRW	WBSel	CSRSEL	CSRWen		
							1 binary digit	3 binary digits	1 binary digit	1 binary digit	1 binary digit	4 binary digits	1 binary digit	2 binary digits	1 binary digit	1 binary digit		
add rd, rs1, rs2	R	0b0110011	0b000	0b00000000	0b0000000	0	1	000	0	0	0	0000	0	01	0	0	8004	
mul rd, rs1, rs2			0b000	0b00000001	0b0000001	1	1	000	0	0	0	1000	0	01	0	0	8104	
sub rd, rs1, rs2			0b000	0b01000000	0b0000010	2	1	000	0	0	0	1100	0	01	0	0	8184	
sll rd, rs1, rs2			0b001	0b00000000	0b0000011	3	1	000	0	0	0	0001	0	01	0	0	8024	
mulh rd, rs1, rs2			0b001	0b00000001	0b0000100	4	1	000	0	0	0	1001	0	01	0	0	8124	
mulhu rd, rs1, rs2			0b011	0b00000001	0b0000101	5	1	000	0	0	0	1011	0	01	0	0	8164	
slt rd, rs1, rs2			0b010	0b00000000	0b0000110	6	1	000	0	0	0	0010	0	01	0	0	8044	
xor rd, rs1, rs2			0b100	0b00000000	0b0000111	7	1	000	0	0	0	0100	0	01	0	0	8084	
srl rd, rs1, rs2			0b101	0b00000000	0b0010000	8	1	000	0	0	0	0101	0	01	0	0	80A4	
sra rd, rs1, rs2			0b101	0b01000000	0b0010001	9	1	000	0	0	0	1101	0	01	0	0	81A4	
or rd, rs1, rs2			0b110	0b00000000	0b0010100	10	1	000	0	0	0	0110	0	01	0	0	80C4	
and rd, rs1, rs2			0b111	0b00000000	0b0010101	11	1	000	0	0	0	0111	0	01	0	0	80E4	
lb rd, offset(rs1)	I	0b0000011	0b000		0b001100	12	1	001	0	0	1	0000	0	00	0	0	9200	
lh rd, offset(rs1)			0b001		0b001101	13	1	001	0	0	1	0000	0	00	0	0	9200	
lw rd, offset(rs1)			0b010		0b001110	14	1	001	0	0	1	0000	0	00	0	0	9200	
addi rd, rs1, imm			0b000		0b001111	15	1	001 [3]	0 [4]	0 [5]	1 [6]	0000	0	01 [7]	0	0	9204	
slli rd, rs1, imm		0b0010011	0b001	0b00000000	0b0100000	16	1	001	0	0	1	0001	0	01	0	0	9224	
slti rd, rs1, imm			0b010		0b010001	17	1	001	0	0	1	0010	0	01	0	0	9244	
xori rd, rs1, imm			0b100		0b010010	18	1	001	0	0	1	0100	0	01	0	0	9284	
srli rd, rs1, imm			0b101	0b00000000	0b010011	19	1	001	0	0	1	0101	0	01	0	0	92A4	
srai rd, rs1, imm			0b101	0b01000000	0b010100	20	1	001	0	0	1	1101	0	01	0	0	93A4	
ori rd, rs1, imm			0b110		0b010101	21	1	001	0	0	1	0110	0	01	0	0	92C4	
andi rd, rs1, imm			0b111		0b010110	22	1	001	0	0	1	0111	0	01	0	0	92E4	
sb rs2, offset(rs1)			S	0b0100011	0b000		0b010111	23	0	010	0	0	1	0000	1	11	0	0
sh rs2, offset(rs1)	0b001				0b011000	24	0	010	0	0	1	0000	1	11	0	0	221C	
sw rs2, offset(rs1)	0b010				0b011001	25	0	010	0	0	1	0000	1	11	0	0	221C	
beq rs1, rs2, offset	0b000				0b011010	26	0	011	0	1	1	0000	0	11	0	0	360C	
bne rs1, rs2, offset	SB	0b1100011	0b001		0b011011	27	0	011	0	1	1	0000	0	11	0	0	360C	
blt rs1, rs2, offset			0b100		0b011100	28	0	011	0	1	1	0000	0	11	0	0	360C	
bge rs1, rs2, offset			0b101		0b011101	29	0	011	0	1	1	0000	0	11	0	0	360C	
bltu rs1, rs2, offset			0b110		0b011110	30	0	011	1	1	1	0000	0	11	0	0	3E0C	
bgeu rs1, rs2, offset			0b111		0b011111	31	0	011	1	1	1	0000	0	11	0	0	3E0C	
auipc rd, offset			U	0b0010111			0b100000	32	1	100	0	1	1	0000	0	01	0	0
lui rd, offset	0b0110111				0b100001	33	1	100	0	0	1	1111	0	01	0	0	C3E4	
jal rd, imm	UJ	0b1101111			0b100010	34	1	101	0	1	1	0000	0	10	0	0	D608	
jalr rd, rs1, imm	I	0b1100111	0b000		0b100011	35	1	001	0	0	1	0000	0	10	0	0	9208	
csrw rd, csr, rs1	CSR	0b1110011	0b001		0b100100	36	0	000	0	0	0	0000	0	11	0	1	000D	
csrw rd, csr, uimm			0b101		0b100101	37	0	110	0	0	0	0000	0	11	1	1	600F	

[1] This is the value that will be passed into the ROM

[2] This is the value that will be outputted from the ROM. It's all the control signals concatenated together.

[3] This value is provided as an example. Based on your design for the immediate generator, you may need to modify this value to generate the correct immediate value

[4] This value actually doesn't matter because the addi instruction never uses the branch comparator. However, you must fill out every cell so the control bits line up properly

[5] This value is provided as an example. Based on your design for the A MUX, you may need to modify this value to generate the correct immediate value

[6] This value is provided as an example. Based on your design for the B MUX, you may need to modify this value to generate the correct immediate value

[7] This value is provided as an example. Based on your design for the Writeback MUX, you may need to modify this value to generate the correct immediate value